

Supplemenatry Exercise on Capacitor(PPC)

Level I

1. (a) $R_1 = 120 \text{ k}\Omega$
 $R_2 = 200 \text{ k}\Omega$
(b) $C_2 = 72.13 \text{ }\mu\text{F}$
2. (a) $3.077 \text{ }\mu\text{C}$, $4.923 \text{ }\mu\text{C}$
(b) both are at $5.54 \times 10^5 \text{ V}$
(c) 0.124 J
3. 0.05 C , 25 J
4. Charge on capacitor $A = 0.036 \text{ C}$
Charge on capacitor $B = 0.072 \text{ C}$
Equivalent capacitance = $900 \text{ }\mu\text{F}$
5. Equivalent capacitance = $1.5 \text{ }\mu\text{F}$
Charge on capacitor $A = 1.5 \text{ mC}$
Charge on capacitor $B = 1.5 \text{ mC}$
6. $8 \text{ }\mu\text{F}$
7. (a) $9.6 \times 10^{-3} \text{ J}$
(b) (i) 53.3 V
(ii) $8.53 \times 10^{-3} \text{ J}$
8. $4 \text{ }\mu\text{F}$

Level II

1. (a) Since the capacitor has been disconnected and isolated, the charge does not change.
 $\therefore Q = CV$
 $= (950 \text{ pF})(400 \text{ V})$
 $= \underline{3.8 \times 10^{-7} \text{ C}}$
(b) $Q = C'V'$
 $\therefore V' = \frac{Q}{C'}$
 $= \frac{3.8 \times 10^{-7}}{50 \times 10^{-12}}$
 $= \underline{7600 \text{ V}}$
(c) Final energy = $\frac{1}{2}QV'$
 $= \frac{1}{2}(3.8 \times 10^{-7})(7600)$
 $= \underline{1.444 \times 10^{-3} \text{ J}}$
(d) Initial energy = $\frac{1}{2}QV$
 $= \frac{1}{2}(3.8 \times 10^{-7})(400)$
 $= 7.6 \times 10^{-5} \text{ J}$
Work done required = final energy – initial energy
 $= \underline{1.368 \times 10^{-3} \text{ J}}$
2. (a) Combined capacitance of $15\text{-}\mu\text{F}$ and $30\text{-}\mu\text{F}$ capacitors = $10 \text{ }\mu\text{F}$
 \therefore Combined capacitance between Z and $B = 10 + 40$
 $= 50 \text{ }\mu\text{F}$
 \therefore p.d. between Z and $B = (240)\left(\frac{50}{50+50}\right)$
 $= \underline{120 \text{ V}}$
(b) For capacitors in series,
 $\frac{V_1}{V_2} = \frac{C_2}{C_1}$
 \therefore p.d. between X and $Y = (120 \text{ V})\left(\frac{15}{15+30}\right)$
 $= \underline{40 \text{ V}}$

(c) If the 50- μF capacitor is shorted,

$$V_{XY} = (240 \text{ V}) \left(\frac{15}{15+30} \right)$$

$$= \underline{80 \text{ V}}$$

(d) We know from part (c) that it will not be the 50- μF capacitor.

If the 30- μF capacitor is shorted, $V_{XY} = 0$.

If the 40- μF capacitor is shorted, $V_{XY} = 0$.

If the 15- μF capacitor is shorted,

combined capacitance between X and Y = $40 + 30$
 $= 70 \mu\text{F}$

$$\therefore V_{XY} = (240 \text{ V}) \left(\frac{50}{50+70} \right)$$

$$= 100 \text{ V}$$

\therefore the 15- μF capacitor is shorted.

3(a) Equivalent capacitance = $\frac{1}{\frac{1}{3} + \frac{1}{2} + \frac{1}{3}}$


$$= \frac{6}{7} \mu\text{F}$$

(b) The equivalent capacitance between X and Y, C_{XY} , can be calculated by using the following equations.

$$\left\{ \begin{array}{l} C = \sum_i C_i \quad \text{for capacitors in parallel} \\ C = \frac{1}{\sum_i \frac{1}{C_i}} \quad \text{for capacitors in series} \end{array} \right.$$

It is found that $C_{XY} = \frac{546}{547} \mu\text{F}$
 $= 0.998 \text{ } 2 \mu\text{F}$

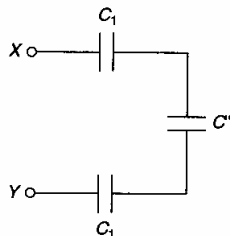(c) The network can be considered as consisting of three capacitors, as shown in the following figure, of which C' has a capacitance equivalent to the remaining six capacitors in Figure 2.29.



Since the three capacitors are connected in series, the charge on each of the capacitors is the same.

$$Q = C_{XY} V_{XY}$$

$$= (0.998 \text{ } 2 \times 10^{-6}) (20)$$

$$= 1.996 \times 10^{-5} \text{ C}$$

4(a) (i) $Q = CV$

$$= (120 \times 10^{-12}) (100)$$

$$= 1.2 \times 10^{-8} \text{ C}$$

(ii) $E = \frac{1}{2} CV^2$

$$= \underline{6 \times 10^{-7} \text{ J}}$$

(b) (i) Let C_1 be the capacitance of the air-filled capacitor and C_2 be the capacitance of the insulator-filled capacitor.

$$\therefore C = \frac{\epsilon A}{d}$$

$$\therefore C_1 = \frac{\epsilon_0 (A/2)}{d}$$

$$= \frac{(\epsilon/6)(A/2)}{d}$$

$$= \frac{1}{12} \left(\frac{\epsilon A}{d} \right)$$

$$= \frac{120 \text{ pF}}{12}$$

$$= 10 \text{ pF}$$

and $C_2 = \frac{\epsilon(A/2)}{d}$

$$= \frac{1}{2} \left(\frac{\epsilon A}{d} \right)$$

$$= \frac{120 \text{ pF}}{2}$$

$$= 60 \text{ pF}$$

$$\therefore \text{combined capacitance} = 10 \text{ pF} + 60 \text{ pF}$$

$$= 70 \text{ pF}$$

(ii) Since the capacitor is isolated, the total charge is constant.

$$Q = 1.2 \times 10^{-8} \text{ C}$$

$$\text{Energy} = \frac{Q^2}{2C}$$

$$= \frac{(1.2 \times 10^{-8})^2}{2(70 \times 10^{-12})}$$

$$= \underline{1.03 \times 10^{-6} \text{ J}}$$

$$\begin{aligned}
 5. \quad (a) \quad (i) \quad Q &= CV \\
 &= (6 \times 10^{-6})(24) \\
 &= \underline{144 \mu\text{C}}
 \end{aligned}$$

(ii) Let q_1 and q_2 be the charges on the 6- μF and 4- μF capacitors respectively.

$$q_1 + q_2 = 144 \quad \dots\dots(1)$$

$$\frac{q_1}{c_1} = \frac{q_2}{c_2}$$

$$\therefore 2q_1 = 3q_2 \quad \dots\dots(2)$$

Solving equations (1) and (2),

$$\begin{aligned}
 q_1 &= 144 \mu\text{C} \times \frac{3}{5} \\
 &= \underline{86.4 \mu\text{C}}
 \end{aligned}$$

$$\begin{aligned}
 q_2 &= 144 \mu\text{C} \times \frac{2}{5} \\
 &= \underline{57.6 \mu\text{C}}
 \end{aligned}$$

$$\begin{aligned}
 (iii) \quad V &= \frac{q_2}{C_2} \\
 &= \frac{57.6 \times 10^{-6}}{4 \times 10^{-6}} \\
 &= \underline{14.4 \text{ V}}
 \end{aligned}$$

(b) Let the new charges on the 6- μF and 2- μF capacitors be Q_1 and Q_2 respectively.

$$Q_1 + Q_2 = 86.4 \mu\text{C} - 57.6 \mu\text{C}$$

$$\therefore Q_1 + Q_2 = 28.8 \mu\text{C} \quad \dots\dots(3)$$

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2}$$

$$2Q_1 = 3Q_2 \quad \dots\dots(4)$$

Solving equations (3) and (4), we get

$$Q_1 = \underline{17.28 \mu\text{C}}$$

$$Q_2 = \underline{11.52 \mu\text{C}}$$