

# Capacitors and

# 20


CHAPTER

1. Charge delivered =  $CV = (10^{-8})(0.18) = 1.8 \times 10^{-9}$  C  
 If this amount is all of the charge in the spoon, then its capacitance =  $1.8 \times 10^{-9} / 10^3 = 1.8$  pF.

Tip: The capacitance of the spoon is only 1/5000 that of the built-in capacitor. Therefore 99.98% of the charge is delivered.

2. (a) Current =  $59 \mu\text{A}$   
 (b) Charge in the capacitor =  $(59 \times 10^{-6})(45) = 2.66 \times 10^{-3}$  C  
 Capacitance =  $2.66 \times 10^{-3} / 5.6 = 470 \mu\text{A}$   
 (c) Current leaking through the voltmeter increases. When it is  $59 \mu\text{A}$ , the voltage becomes steady.  
 $I/20 \times 10^3 = 59 \times 10^{-6}$   
 $V = 1.18$  V
3. (a) Charge on the capacitor at 1 s =  $(59 \times 10^{-6})(1) = 59 \times 10^{-6}$  C  
 Voltage =  $59 \times 10^{-6} / 470 \times 10^{-6} = 0.126$  V  
 Vertical deflection = 0.126 div  
 (b) Charge stored at 20 s =  $(59 \times 10^{-6})(20) = 1.18 \times 10^{-3}$  C  
 (c) Voltage of capacitor =  $(0.126)(20) = 2.52$  V  
 $R = (6 - 2.52) / 59 \times 10^{-6} = 5.9 \times 10^4 \Omega$   
 (d) When the voltage of the capacitor reaches 6 V, a steady current cannot be sustained.  
 Charge in the capacitor at 6 V =  $(6)(470 \times 10^{-6}) = 2.82 \times 10^{-3}$  C  
 Time of charging =  $2.82 \times 10^{-3} / 59 \times 10^{-6} = 47.8$  s

(e)

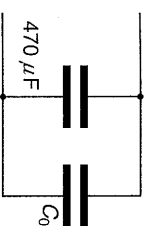


Equivalent capacitance =  $470 \times 10^{-6} + C_0$  (from the diagram)

If the measured voltage is  $V$ , then  $Q$  is  $470 \times 10^{-6} V$ , but in fact  $Q$  should be  $(470 \times 10^{-6} + C_0)V$ .

Thus, a factor of  $C_0 / 470 \times 10^{-6}$  should be added to the observed voltage.

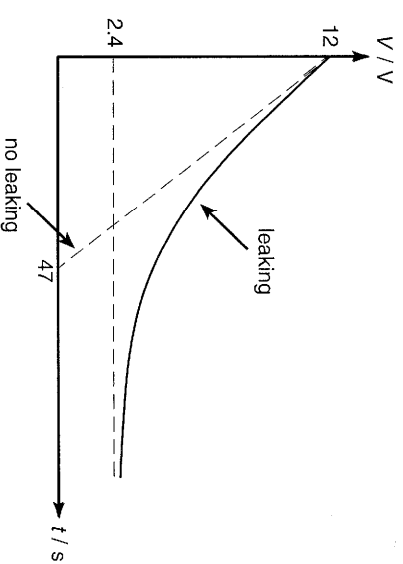4. (a) If there is no leakage, the relationship between  $R$  and  $t$  is given by  $12 - Q/C = IR$  with  $Q = It$  and  $V = IR$ .  
 $V = 12 - (120 \times 10^{-6} / 470 \times 10^{-6})t = 12 - (12/47)t$   
 At  $t = 47$  s,  $V$  should be zero.




- (b) Final voltage of capacitor =  $12 - 2.4 = 9.6$  V  
 Final charge stored =  $(9.6)(470 \times 10^{-6}) = 4.5 \times 10^{-3}$  C  
 (c) The charge in the capacitor remains constant when the voltage across the capacitor remains constant. All of the  $120 \mu\text{A}$  current leaks through the capacitor.  
 $\therefore$  Leakage resistance =  $9.6 / 120 \times 10^{-6} = 80 \text{ k}\Omega$
5. (a) Since  $C = \epsilon_0 A / d$ ,  $A$  decreases as  $C$  decreases.  $V$  ( $= Q / C$ ) will increase. The capacitor discharges and the pointer 'kicks' in the opposite direction.  
 (b) Since  $C = \epsilon \epsilon_0 A / d$ , inserting a dielectric sheet increases  $C$ .  $V$  then decreases and more charge flows into the capacitor. The pointer 'kicks' in the original direction.


6.  $C = \epsilon_0 A / d = (6)(8.85 \times 10^{-12})(100 \times 10^{-4}) / 0.1 \times 10^{-3} = 5.3 \times 10^3 \text{ pF}$

Tip: The answer is seldom written as  $5.3 \times 10^{-9} \text{ F}$ . The two commonly used units of capacitance are  $\mu\text{F}$  or  $\text{pF}$ , thus write it as  $5.3 \times 10^{-3} \mu\text{F}$  or  $5.3 \times 10^3 \text{ pF}$ .


7. (a)

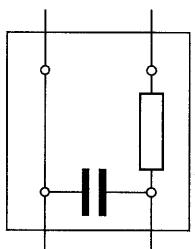


(b)

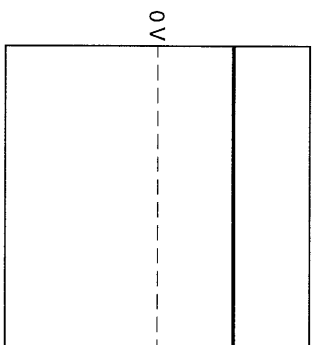


(c)

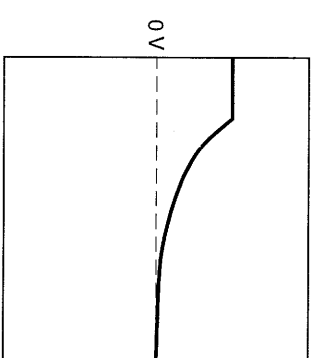

8. (a)

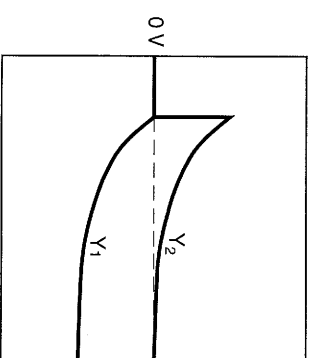

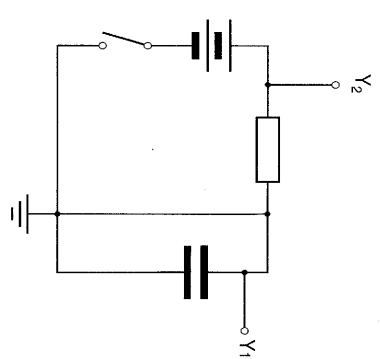(b) If  $Y_1$  and E are interchanged, the capacitance is shorted and the circuit is as shown in the diagram.



$Y_1 = 0$  and  $Y_2 =$  voltage of the battery

Tip: Thus, there are restrictions on the connections of  $Y_1$ ,  $Y_2$  and E when using a double-beam CRO.

9. (a) Initial charge =  $CV_0 = (470 \times 10^{-6})(4.7) = 2.2 \times 10^{-3} \text{ C}$

(b) From the figure,  $Q$  drops to  $1/e$  of its original value in 28 s.  
 $RC = 28$   
 $R = 28 / 470 \times 10^{-6} = 5.96 \times 10^4 \Omega$

10. (a) Increase  $Q_0$ .  $I_0 = Q_0 C / R$

(b) Increase  $C$ .  $I_0 = V_0 / R = V_0 C^2 \sqrt{2} / (RC \sqrt{2}) = V_0 C^2 \sqrt{2} / t_{1/2}$

11. (a) Time of discharge =  $(1 / 400) / 2 = 1.25 \times 10^{-3} \text{ s}$

Time constant of the RC circuit =  $(580 \times 10^{-12})(10 \times 10^6) = 5.8 \times 10^{-3} \text{ s}$   
 $V = V_0 \exp(-t / RC) = 20.15 \text{ V}$

(b) Current registered = charge passed through in 1 s  
 $= (400)(25 - 20.15)(580 \times 10^{-12}) = 1.13 \mu\text{A}$

(c)  $\exp(-t / RC) = (V_0 - V) / V_0 = 1 - 0.99$   
 $t / RC = 4.61$  with  $t = 1.25 \times 10^{-3}$   
 $R = 470 \text{ k}\Omega$


12. Time of discharge =  $0.5 \times 10^{-3}$  s  
 Minimum value of  $RC = (400 \times 10^3)(580 \times 10^{-12}) = 2.32 \times 10^{-4}$  s  
 $\therefore$  Time of discharge =  $2.2 RC$

Fraction of charge left =  $\exp(-2.2) = 0.11$

A switching frequency of 1 kHz is not practical since only 89% of the charge would be discharged.


13. (a) Time of charging =  $(1/50)/2 = 10$  ms  
 Time constant of the charging circuit =  $(2 \times 10^{-6})(5 \times 10^3) = 10$  ms  
 $V = 6 \exp[(1 - (1/e))] = 3.8$  V

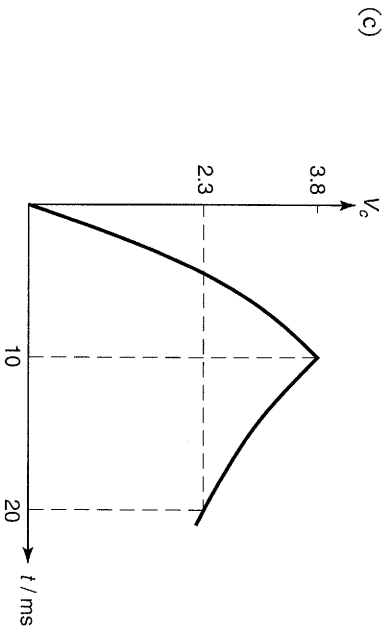- (b) Time constant of the discharging circuit =  $(2 \times 10^{-6})(10^4) = 20$  ms  
 $V = 3.8 \exp(-10/20) = 2.3$  V



14. (a) Time constant of the circuit =  $(4700 \times 10^{-6})(10^4) = 47$  s  
 $Q = (4700 \times 10^{-6})(9) \exp(-20/47) = 2.76 \times 10^{-2}$  C  
 (b)  $V = Q/C = 5.88$  V  
 (c)  $V_R = V_C = 5.88$  V  
 (d)  $I = 5.88/(10 \times 10^3) = 588 \mu\text{A}$

15. (a)

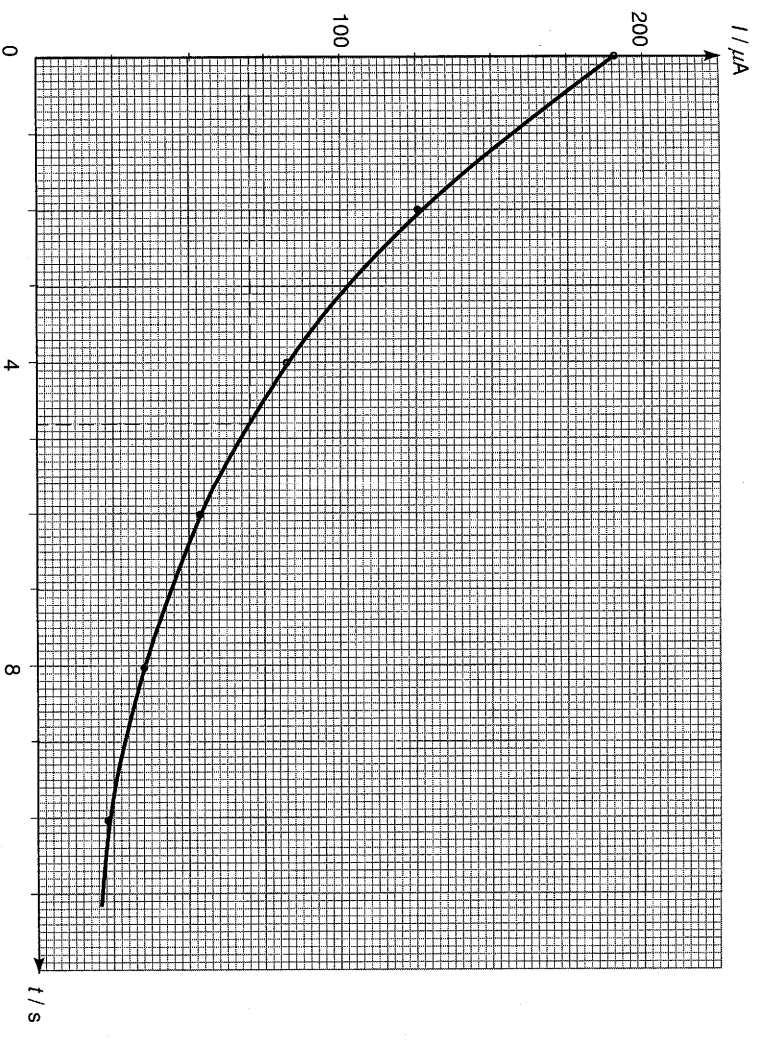

- (b) The time for the current to fall to  $1/e$  of the initial value, i.e. when  $I = 0.37 \times 190 = 70 \mu\text{A}$ , is 4.8 s.  
 $\therefore C = 4.8/R = 102 \mu\text{F}$


- (c)  $R$  must be ten-times larger for the time constant to be measurable.

16. (a) Initial current =  $25/500 = 50$  mA  
 (b) Time for the initial current to drop to 10 mA is  $t_2$  where  $t$  is given by  $10 = 50 \exp(-t/RC)$ .  
 $t = (1.61)(500)(4700 \times 10^{-6}) = 3.8$  s

17. (a) Equivalent capacitance of the  $100 \mu\text{F}$  and the  $220 \mu\text{F}$  capacitors =  $100 + 220 = 320 \mu\text{F}$   
 Equivalent capacitance of the  $320 \mu\text{F}$  capacitor and the  $470 \mu\text{F}$  capacitor =  $[(320 \times 10^{-6})^{-1} + (470 \times 10^{-6})^{-1}]^{-1} = 190 \mu\text{F}$


- (b) Voltage ratio of the 470 and 320  $\mu\text{F}$  capacitors =  $320 / 470$ .  
 Sum of the two voltages = 6 V  
 Voltage across the 470  $\mu\text{F}$  capacitor =  $(6)(320)/(320 + 470) = 2.43$  V  
 Voltage across the 220  $\mu\text{F}$  capacitor = 3.57 V  
 Energy =  $CV^2 / 2$ , thus the energy stored in the 100, 220 and 470  $\mu\text{F}$  capacitors is respectively 0.64 mJ, 1.40 mJ and 1.39 mJ.

18.

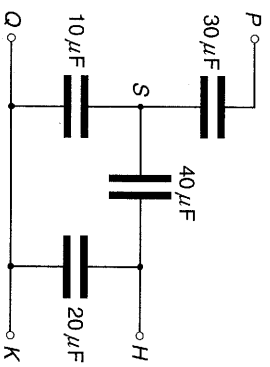

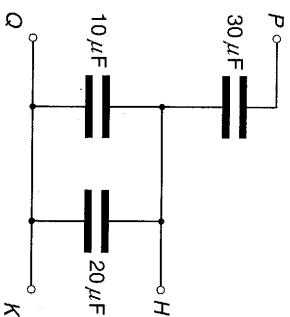
- (a) Equivalent capacitance of the 40 and 20  $\mu\text{F}$  capacitors  
 $= [(40 \times 10^{-6})^{-1} + (20 \times 10^{-6})^{-1}] = 13.3 \mu\text{F}$   
 Equivalent capacitance between  $SQ = 13.3 + 10 = 23.3 \mu\text{F}$   
 $V_{rs} / V_{sq} = 23.3 / 30$  and  $V_{pq} = 600$  V  
 $V_{sq} = 338$  V  
 $V_{sh} / V_{hk} = 20 / 40$  and  $V_{sk} = 338$  V  
 $V_{hk} = 225.3$  V  
 (b) The 40  $\mu\text{F}$  capacitor.

Tip: In (b), the equivalent circuit is shown.  
 Verify that  $V_{HK} = 300$  V.




30

19. (a)

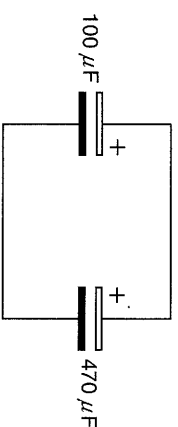

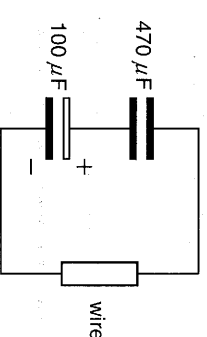
- (b) Total charge =  $(100 \times 10^{-6})(9) = 900 \mu\text{C}$   
 Final charge on the 100  $\mu\text{F}$  capacitor  
 $= (100 / 570)(900 \times 10^{-6})$   
 $= 158 \mu\text{C}$   
 Final charge on the 470  $\mu\text{F}$  capacitor  
 $= 900 - 158$   
 $= 742 \mu\text{C}$   
 (c) P.d. across the capacitor  
 $= 158 \times 10^{-6} / 100 \times 10^{-6}$   
 $= 1.58$  V  
 (d) Energy stored in the 100  $\mu\text{F}$  capacitor  
 $= (158 \times 10^{-6})(1.58)$   
 $= 125 \mu\text{J}$   
 Energy stored in the 470  $\mu\text{F}$  capacitor  
 $= (742 \times 10^{-6})^2 / 470 \times 10^{-6}$   
 $= 586 \mu\text{J}$   
 (e) Equivalent capacitance =  $[(100 \times 10^{-6})^{-1} + (470 \times 10^{-6})^{-1}] = 82.5 \mu\text{F}$   
 Time constant =  $(0.1)(82.5 \times 10^{-6}) = 8.25 \times 10^{-6}$  s  
 It takes about  $5RC$  to complete the discharge, i.e.  $\sim 40 \times 10^{-3}$  s  
 (f) Some energy is dissipated in resistive heating in the wire.

Tip: The figure shows the equivalent circuit in (e).



31

20. (a)

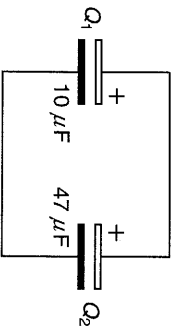

$$Q_{10} = (10 \times 10^{-6})(9) = 90 \mu\text{C}$$

$$Q_{20} = (47 \times 10^{-6})(6) = 282 \mu\text{C}$$

$$\text{Total charge} = 372 \mu\text{C}$$

At equilibrium,  $Q_1 / Q_2 = 10 / 47$

$$Q_1 = 65 \mu\text{C}, Q_2 = 307 \mu\text{C}$$

$$V_1 = V_2 = 65 \times 10^{-6} / 10 \times 10^{-6} = 6.5 \text{ V}$$

$$\text{Initial energy} = [90 \times 10^{-6}(9) + (282 \times 10^{-6})(6)] / 2$$

$$= 1.251 \times 10^{-3} \text{ J}$$

$$\text{Final energy} = (372 \times 10^{-6})(6.5) / 2$$

$$= 1.209 \times 10^{-3} \text{ J}$$

$$\text{Energy dissipated} = 42 \mu\text{J}$$

(b) Total charge = 282 - 90 = 192  $\mu\text{C}$

$$Q_1 = (10 / 57)(192) = 33.7 \mu\text{C}$$

$$Q_2 = 192 - 33.7 = 158.3 \mu\text{C}$$

$$V_1 = V_2 = 33.7 \times 10^{-6} / 10 \times 10^{-6} = 3.37 \text{ V}$$

$$\text{Final energy} = (192 \times 10^{-6})(3.37) / 2$$

$$= 0.3235 \times 10^{-3} \text{ J}$$

$$\text{Energy dissipated} = 930 \mu\text{J}$$

21. (a)

When it is fully charged, the voltage across it is 9 V.

$$\text{Energy stored} = \int V dQ = \int (Q / C) dQ = Q^2 / 2C = CV^2 / 2$$

$$= (4700 \times 10^{-6})(9)^2 / 2 = 0.19 \text{ J}$$

(b) Energy dissipated in resistor =  $R \int I^2 dt = (V^2 / R) \int \exp(-2t / RC) dt$

$$= V^2 C / 2 = 0.19 \text{ J}$$

(c) Total energy output =  $QV = QC^2 = 0.38 \text{ J}$

Tip: Note the relationships among the results of the three parts.